

ASSIGNMENT 4

Name: - Meet Chetankumar Soni

ID NO.: - 21EL035

Division: - 04

Year: - 2023-24

Subject: - Digital System Design (3EL42)

Branch: - Electronics (EL)

Q1. BCD Time Count


Verilog Code:

```
////////////////////////////////////  
module bcd_Count(  
    input clock, reset,  
    output reg [3:0]dout  
);  
    initial dout = 0;  
  
    always @ (posedge (clock))  
    begin  
        if (reset)  
            dout <= 0;  
        else if (dout <= 9)  
            dout <= dout + 1;  
        else if (dout == 9)  
            dout <= 0;  
    end  
endmodule
```

Test Bench:

```
module bcdcounter_testbench();  
    reg clock, reset;  
    wire [3:0] dout;  
  
    bcd_counter dut(clock, reset, dout);  
    initial begin  
        clock=0;  
        forever #5 clock=~clock;  
    end  
    initial begin  
        reset=1;  
        #20;  
        reset=0;  
    end  
endmodule
```

RTL Schematic:

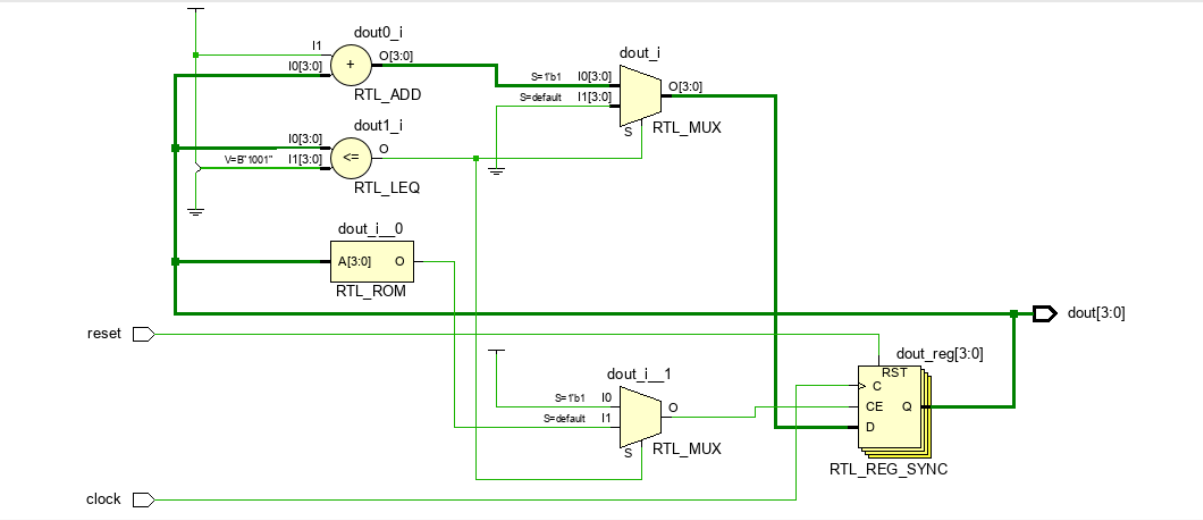

Synthesis Report:

```
-----
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+-----+
| BlackBox name | Instances |
+-----+-----+

Report Cell Usage:
+-----+-----+
| Cell | Count |
+-----+-----+
|1| BUFG | 1|
|2| LUT3 | 1|
|3| LUT4 | 4|
|4| FDRE | 4|
|5| IBUF | 2|
|6| OBUF | 4|
+-----+-----+

Report Instance Areas:
+-----+-----+
| Instance | Module | Cells |
+-----+-----+
|1| top | | 16|
+-----+-----+

Finished Writing Synthesis Report : Time (s): cpu = 00:00:18 ; elapsed = 00:00:22 . Memory (MB): peak = 1019.316 ; gain = 0.000
-----
```


Power Report:

Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power:	2.855 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	30.4°C
Thermal Margin:	54.6°C (28.8 W)
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

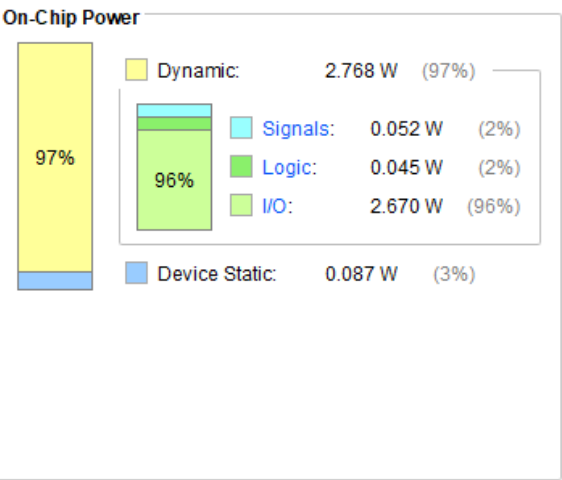[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



Q2.3-1 MUX


Verilog Code:

```
module mux_2_1(  
    input sel,  
    input i0, i1,  
    output y);  
  
    assign y = sel ? i1 : i0;  
endmodule  
  
module mux_3_1(  
    input sel0, sel1,  
    input i0,i1,i2,i3,  
    output reg y);  
  
    wire y0, y1;  
  
    mux_2_1 m1(sel1, i0, i1, y0);  
    mux_2_1 m2(sel0, y0, i2, y);  
endmodule
```

Test Bench:

```
module tb;  
    reg sel0, sel1;  
    reg i0,i1,i2,i3;  
    wire y;  
  
    mux_3_1 mux(sel0, sel1, i0, i1, i2, i3, y);  
  
    initial begin  
        $monitor("sel0=%b, sel1=%b -> i3 = %0b, i2 = %0b ,i1 = %0b, i0 = %0b -> y = %0b", sel0,sel1,i3,i2,i1,i0, y);  
        {i3,i2,i1,i0} = 4'h5;  
  
        repeat(8) begin  
            {sel0, sel1} = $random;  
            #5;  
        end  
    end  
endmodule
```

RTL Schematic:

 

Synthesis Report:

```
-----
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+
| BlackBox name |Instances |
+-----+
+-----+

Report Cell Usage:
+-----+
| Cell |Count |
+-----+
|1 |LUT5 | 1|
|2 |IBUF | 5|
|3 |OBUF | 1|
+-----+

Report Instance Areas:
+-----+
| Instance |Module |Cells |
+-----+
|1 |top | | 7|
+-----+

-----
Finished Writing Synthesis Report : Time (s): cpu = 00:00:18 ; elapsed = 00:00:25 . Memory (MB): peak = 1014.996 ; gain = 0.000
-----
```

Power Report:

Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power:	0.49 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	25.9°C
Thermal Margin:	59.1°C (31.2 W)
Effective θJA:	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

Dynamic:	0.408 W	(83%)
Device Static:	0.082 W	(17%)

Signals:	0.011 W	(3%)
Logic:	0.003 W	(1%)
I/O:	0.394 W	(96%)

Q3. BCD to Seven Segment Display


Verilog Code:

```
///////////////////////////////////////////////////  
module segment7(  
    bcd,  
    seg  
);  
  
    //Declare inputs,outputs and internal variables.  
    input [3:0] bcd;  
    output [6:0] seg;  
    reg [6:0] seg;  
  
    //always block for converting bcd digit into 7 segment format  
    always @(bcd)  
    begin  
        case (bcd) //case statement  
            0 : seg = 7'b0000001;  
            1 : seg = 7'b1001111;  
            2 : seg = 7'b0010010;  
            3 : seg = 7'b0000110;  
            4 : seg = 7'b1001100;  
            5 : seg = 7'b0100100;  
            6 : seg = 7'b0100000;  
            7 : seg = 7'b0001111;  
            8 : seg = 7'b0000000;  
            9 : seg = 7'b0000100;  
            //switch off 7 segment character when the bcd digit is not a decimal number.  
            default : seg = 7'b1111111;  
        endcase  
    end  
endmodule
```

Test Bench:

```
module tb_segment7;  
  
    reg [3:0] bcd;  
    wire [6:0] seg;  
    integer i;  
  
    // Instantiate the Unit Under Test (UUT)  
    segment7 uut (  
        .bcd(bcd),  
        .seg(seg)  
    );  
  
    //Apply inputs  
    initial begin  
        for(i = 0;i < 16;i = i+1) //run loop for 0 to 15.  
        begin  
            bcd = i;  
            #10; //wait for 10 ns  
        end  
    end  
endmodule
```

RTL Schematic:

 

Synthesis Report:

```
-----
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+-----+
| BlackBox name | Instances |
+-----+-----+

Report Cell Usage:
+-----+-----+
| Cell | Count |
+-----+-----+
| 1 | LUT4 | 7 |
| 2 | IBUF | 4 |
| 3 | OBUF | 7 |
+-----+-----+

Report Instance Areas:
+-----+-----+
| Instance | Module | Cells |
+-----+-----+
| 1 | top | | 18 |
+-----+-----+

Finished Writing Synthesis Report : Time (s): cpu = 00:00:15 ; elapsed = 00:00:17 . Memory (MB): peak = 1016.211 ; gain = 0.000
-----
```


Power Report:

Summary	
Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.	
Total On-Chip Power:	2.767 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	30.2°C
Thermal Margin:	54.8°C (28.9 W)
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low
Launch Power Constraint Advisor to find and fix invalid switching activity	
<div><div>On-Chip Power</div><div><div><div>97%</div></div><div><div>Dynamic: 2.680 W (97%)</div><div><div>96%</div><div>Signals: 0.074 W (3%)</div><div>Logic: 0.022 W (1%)</div><div>I/O: 2.585 W (96%)</div></div></div><div>Device Static: 0.087 W (3%)</div></div></div>	

Q4. D Latch using 2:1 MUX

Verilog Code:

```
module DFFusingMUX(input d1, d0, sel, clk, rst, output reg q);
    reg d;

    always @ (*)
    begin
        case(sel)
            0 : d = d0;
            1 : d = d1;
        endcase
    end

    always @(posedge clk)
    begin
        if(rst)
            q <= 0;
        else
            q <= d;
        end
    end
endmodule
```

Test Bench:

```
module tb;
    reg d1,d0;
    reg clk;
    reg rst;
    wire q;


    d_latch d3(q,d1,d0,clk,rst);

    initial
    begin
        clk = 1'b0;
        forever #20 clk = ~clk ;
    end

    initial
    begin
        rst = 1'b1;
        #40;
        rst = 1'b0;
        #40;
        d0 = 1'b0;
        d1= 1'b0;
        #40
        d0 = 1'b1;
        d1 = 1'b0;
        #40;

        $finish ;
    end
endmodule
```

RTL Schematic:

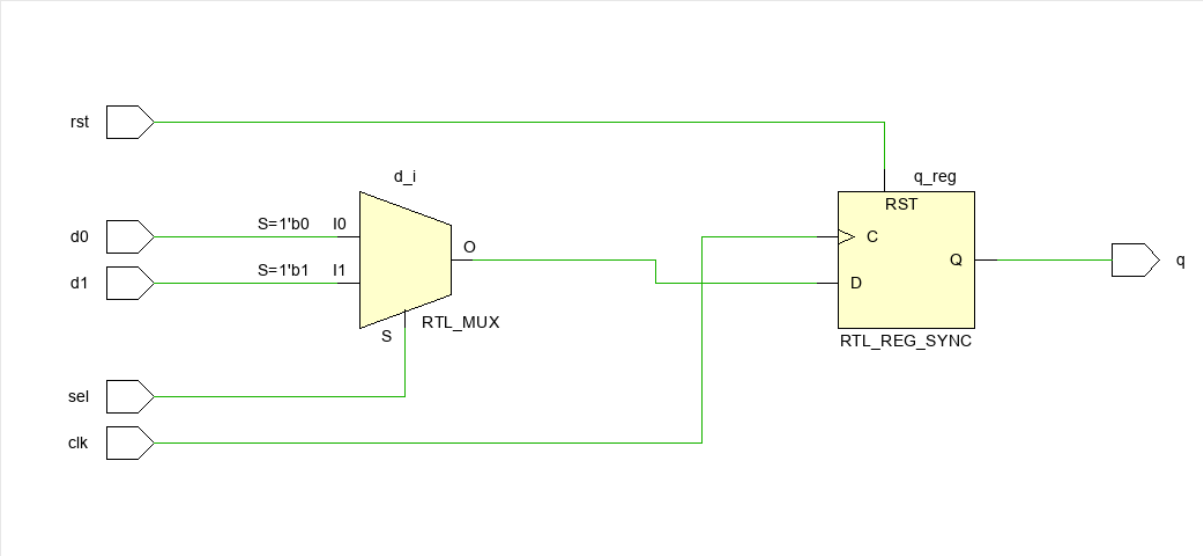

Synthesis Report:

```
-----
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+
| BlackBox name | Instances |
+-----+
+-----+

Report Cell Usage:
+-----+
| Cell | Count |
+-----+
|1| BUFG | 1|
|2| LUT13 | 1|
|3| FDRE | 1|
|4| IBUF | 5|
|5| OBUF | 1|
+-----+

Report Instance Areas:
+-----+
| Instance | Module | Cells |
+-----+
|1| top | | 9|
+-----+

-----
Finished Writing Synthesis Report : Time (s): cpu = 00:00:14 ; elapsed = 00:00:20 . Memory (MB): peak = 1019.727 ; gain = 0.000
-----
```

Power Report:

Summary	
Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.	
Total On-Chip Power:	0.457 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	25.9°C
Thermal Margin:	59.1°C (31.2 W)
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low
Launch Power Constraint Advisor to find and fix invalid switching activity	
On-Chip Power	
Dynamic: 0.375 W (82%)	
Device Static: 0.082 W (18%)	
Signals: 0.012 W (3%)	
Logic: 0.009 W (2%)	
I/O: 0.355 W (95%)	

Q5. 8-BIT Barrel Shifter

Verilog Code:

```
module barrel_shifter_8bit (in, ctrl, out);
    input [7:0] in;
    input [2:0] ctrl;
    output [7:0] out;
    wire [7:0] x,y;

    //4bit shift right
    mux2X1 ins_17 (.in0(in[7]),.in1(1'b0),.sel(ctrl[2]),.out(x[7]));
    mux2X1 ins_16 (.in0(in[6]),.in1(1'b0),.sel(ctrl[2]),.out(x[6]));
    mux2X1 ins_15 (.in0(in[5]),.in1(1'b0),.sel(ctrl[2]),.out(x[5]));
    mux2X1 ins_14 (.in0(in[4]),.in1(1'b0),.sel(ctrl[2]),.out(x[4]));
    mux2X1 ins_13 (.in0(in[3]),.in1(in[7]),.sel(ctrl[2]),.out(x[3]));
    mux2X1 ins_12 (.in0(in[2]),.in1(in[6]),.sel(ctrl[2]),.out(x[2]));
    mux2X1 ins_11 (.in0(in[1]),.in1(in[5]),.sel(ctrl[2]),.out(x[1]));
    mux2X1 ins_10 (.in0(in[0]),.in1(in[4]),.sel(ctrl[2]),.out(x[0]));

    //2 bit shift right

    mux2X1 ins_27 (.in0(x[7]),.in1(1'b0),.sel(ctrl[1]),.out(y[7]));
    mux2X1 ins_26 (.in0(x[6]),.in1(1'b0),.sel(ctrl[1]),.out(y[6]));
    mux2X1 ins_25 (.in0(x[5]),.in1(x[7]),.sel(ctrl[1]),.out(y[5]));
    mux2X1 ins_24 (.in0(x[4]),.in1(x[6]),.sel(ctrl[1]),.out(y[4]));
    mux2X1 ins_23 (.in0(x[3]),.in1(x[5]),.sel(ctrl[1]),.out(y[3]));
    mux2X1 ins_22 (.in0(x[2]),.in1(x[4]),.sel(ctrl[1]),.out(y[2]));
    mux2X1 ins_21 (.in0(x[1]),.in1(x[3]),.sel(ctrl[1]),.out(y[1]));
    mux2X1 ins_20 (.in0(x[0]),.in1(x[2]),.sel(ctrl[1]),.out(y[0]));

    //1 bit shift right
    mux2X1 ins_07 (.in0(y[7]),.in1(1'b0),.sel(ctrl[0]),.out(out[7]));
    mux2X1 ins_06 (.in0(y[6]),.in1(y[7]),.sel(ctrl[0]),.out(out[6]));
    mux2X1 ins_05 (.in0(y[5]),.in1(y[6]),.sel(ctrl[0]),.out(out[5]));
    mux2X1 ins_04 (.in0(y[4]),.in1(y[5]),.sel(ctrl[0]),.out(out[4]));
    mux2X1 ins_03 (.in0(y[3]),.in1(y[4]),.sel(ctrl[0]),.out(out[3]));
    mux2X1 ins_02 (.in0(y[2]),.in1(y[3]),.sel(ctrl[0]),.out(out[2]));

    //2 bit shift right

    mux2X1 ins_27 (.in0(x[7]),.in1(1'b0),.sel(ctrl[1]),.out(y[7]));
    mux2X1 ins_26 (.in0(x[6]),.in1(1'b0),.sel(ctrl[1]),.out(y[6]));
    mux2X1 ins_25 (.in0(x[5]),.in1(x[7]),.sel(ctrl[1]),.out(y[5]));
    mux2X1 ins_24 (.in0(x[4]),.in1(x[6]),.sel(ctrl[1]),.out(y[4]));
    mux2X1 ins_23 (.in0(x[3]),.in1(x[5]),.sel(ctrl[1]),.out(y[3]));
    mux2X1 ins_22 (.in0(x[2]),.in1(x[4]),.sel(ctrl[1]),.out(y[2]));
    mux2X1 ins_21 (.in0(x[1]),.in1(x[3]),.sel(ctrl[1]),.out(y[1]));
    mux2X1 ins_20 (.in0(x[0]),.in1(x[2]),.sel(ctrl[1]),.out(y[0]));

    //1 bit shift right
    mux2X1 ins_07 (.in0(y[7]),.in1(1'b0),.sel(ctrl[0]),.out(out[7]));
    mux2X1 ins_06 (.in0(y[6]),.in1(y[7]),.sel(ctrl[0]),.out(out[6]));
    mux2X1 ins_05 (.in0(y[5]),.in1(y[6]),.sel(ctrl[0]),.out(out[5]));
    mux2X1 ins_04 (.in0(y[4]),.in1(y[5]),.sel(ctrl[0]),.out(out[4]));
    mux2X1 ins_03 (.in0(y[3]),.in1(y[4]),.sel(ctrl[0]),.out(out[3]));
    mux2X1 ins_02 (.in0(y[2]),.in1(y[3]),.sel(ctrl[0]),.out(out[2]));
    mux2X1 ins_01 (.in0(y[1]),.in1(y[2]),.sel(ctrl[0]),.out(out[1]));
    mux2X1 ins_00 (.in0(y[0]),.in1(y[1]),.sel(ctrl[0]),.out(out[0]));

endmodule

////////////////////////
//2X1 Mux
////////////////////////

module mux2X1( in0,in1,sel,out);
    input in0,in1;
    input sel;
    output out;
    assign out=(sel)?in1:in0;
endmodule
```

Test Bench:

```


) module barrel_shifter_8bit_tb;
    reg [7:0] in;
    reg [2:0] ctrl;
    wire [7:0] out;

    barrel_shifter_8bit uut(.in(in), .ctrl(ctrl), .out(out));

) initial
) begin
    $display($time, " << Starting the Simulation >>");
    in= 8'd0; ctrl=3'd0; //no shift
    #10 in=8'd128; ctrl= 3'd4; //shift 4 bit
    #10 in=8'd128; ctrl= 3'd2; //shift 2 bit
    #10 in=8'd128; ctrl= 3'd1; //shift by 1 bit
    #10 in=8'd255; ctrl= 3'd7; //shift by 7bit
) end
) initial begin
    $monitor("Input=%d, Control=%d, Output=%d",in,ctrl,out);
) end
) endmodule

```

RTL Schematic:

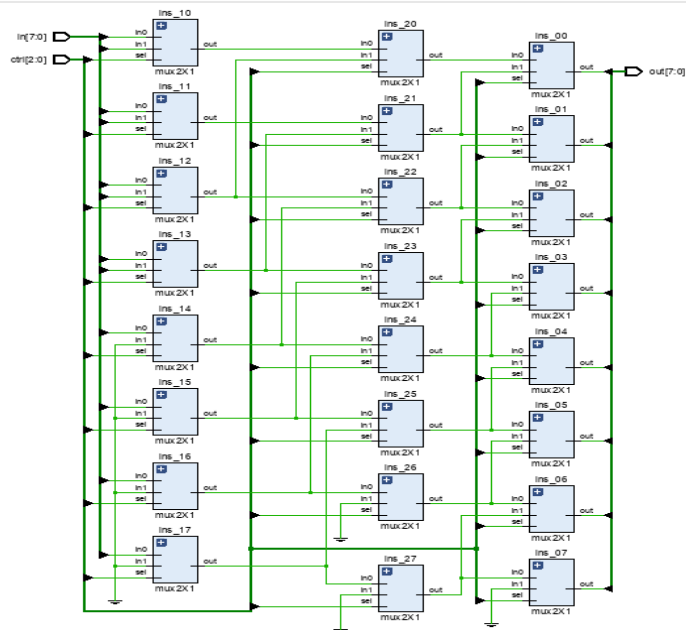

Synthesis Report:

```
-----
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+
| BlackBox name |Instances |
+-----+
+-----+

Report Cell Usage:
+-----+
| Cell |Count |
+-----+
|1| LUT3 | 3|
|2| LUT4 | 2|
|3| LUT5 | 3|
|4| LUT6 | 5|
|5| IBUF | 11|
|6| OBUF | 8|
+-----+

Report Instance Areas:
+-----+
| Instance |Module |Cells |
+-----+
|1| top | | 32|
+-----+

-----
Finished Writing Synthesis Report : Time (s): cpu = 00:00:13 ; elapsed = 00:00:16 . Memory (MB): peak = 1020.242 ; gain = 0.000
-----
```

Power Report:

Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power:	2.904 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	30.5°C
Thermal Margin:	54.5°C (28.8 W)
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

Dynamic:	2.817 W	(97%)
Signals:	0.132 W	(5%)
Logic:	0.045 W	(2%)
I/O:	2.639 W	(93%)
Device Static:	0.087 W	(3%)

Q6. 1-BIT Comparator using 4X1 MUX


Verilog Code:

```
//////////////////////////////////////////  
module comp_lbit(out, a, b, c, d, s0, s1);  
  
    output out;  
    input a, b, c, d, s0, s1;  
    wire sobar, slbar, T1, T2, T3, T4;  
  
    not (s0bar, s0), (slbar, s1);  
    and (T1, a, s0bar, slbar), (T2, b, s0bar, s1), (T3, c, s0, slbar), (T4, a, s0, s1);  
    or(out, T1, T2, T3, T4);  
  
endmodule
```

Test Bench:

```
.....  
) module tb;  
  
    wire out;  
    reg a;  
    reg b;  
    reg c;  
    reg d;  
    reg s0, s1;  
  
    m41 name(.out(out), .a(a), .b(b), .c(c), .d(d), .s0(s0), .s1(s1));  
) initial  
) begin  
  
    a=1'b0; b=1'b0; c=1'b0;  
    s0=1'b0; s1=1'b0;  
    #500 $finish;  
  
) end  
  
    always #40 a=~a;  
    always #20 b=~b;  
    always #10 c=~c;  
    always #80 s0=~s0;  
    always #160 s1=~s1;  
  
) always@(a or b or c or s0 or s1)  
) $monitor("At time = %t, Output = %d", $time, out);  
  
) endmodule
```


RTL Schematic:

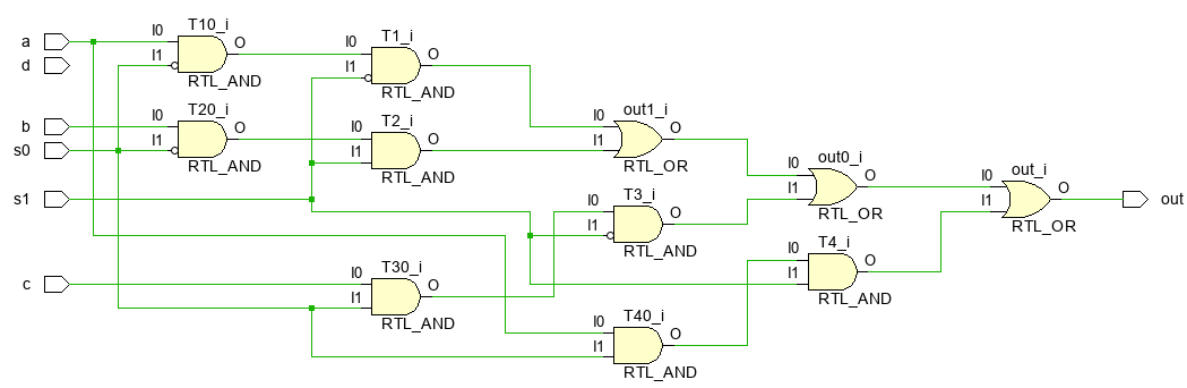

Synthesis Report:

```
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+
| BlackBox name |Instances |
+-----+
+-----+

Report Cell Usage:
+-----+
| Cell |Count |
+-----+
|1 |LUT5 | 1|
|2 |IBUF | 5|
|3 |OBUF | 1|
+-----+

Report Instance Areas:
+-----+
| Instance |Module |Cells |
+-----+
|1 |top | | 7|
+-----+

Finished Writing Synthesis Report : Time (s): cpu = 00:00:24 ; elapsed = 00:00:37 . Memory (MB): peak = 1021.613 ; gain = 0.000
-----
```

Power Report:

Summary	
Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.	
Total On-Chip Power:	0.531 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	26.0°C
Thermal Margin:	59.0°C (31.1 W)
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low
Launch Power Constraint Advisor to find and fix invalid switching activity	
On-Chip Power	
Dynamic: 0.449 W (85%)	
Signals: 0.012 W (3%)	
Logic: 0.004 W (1%)	
I/O: 0.434 W (96%)	
Device Static: 0.082 W (15%)	

Q7.Logical, Algebraic, and Rotate Shift Operations

Verilog Code:

```
) module shift_rotate (a, opcode, result);
  input [7:0] a;
  input [2:0] opcode;
  output [7:0] result;
  wire [7:0] a;
  wire [2:0] opcode;
  reg [7:0] result;

  parameter sra_op = 3'b000,
    srl_op = 3'b001,
    sla_op = 3'b010,
    sll_op = 3'b011,
    ror_op = 3'b100,
    rol_op = 3'b101;

  always @ (a or opcode)
  begin
    case (opcode)
    ) sra_op : result = {a[7], a[7], a[6], a[5],
    ) a[4], a[3], a[2], a[1]};
    ) srl_op : result = a >> 1;
    ) sla_op : result = {a[6], a[5], a[4], a[3],
    ) a[2], a[1], a[0], 1'b0};
    ) sll_op : result = a << 1;
    ) ror_op : result = {a[0], a[7], a[6], a[5],
    ) a[4], a[3], a[2], a[1]};
    ) rol_op : result = {a[6], a[5], a[4], a[3],
    ) a[2], a[1], a[0], a[7]};
    default : result = 0;
    ) endcase
  ) end
) endmodule
```

Test Bench:

```

module shift_rotate_tb;

    reg [7:0] a;
    reg [2:0] opcode;
    wire [7:0] result;
    integer i;
    shift_rotate uut (
        .a(a),
        .opcode(opcode),
        .result(result)
    );

    initial begin
        a=8'b10110101;
        opcode = 000;

        end


    initial
    begin
        for(i=0;i<6;i=i+1)
        begin
            opcode=i;
            #10;
        end
    end

    initial
    $monitor(" A=%b | Opcode=%b | Result =%b ",a,opcode,result);

endmodule

```

RTL Schematic:

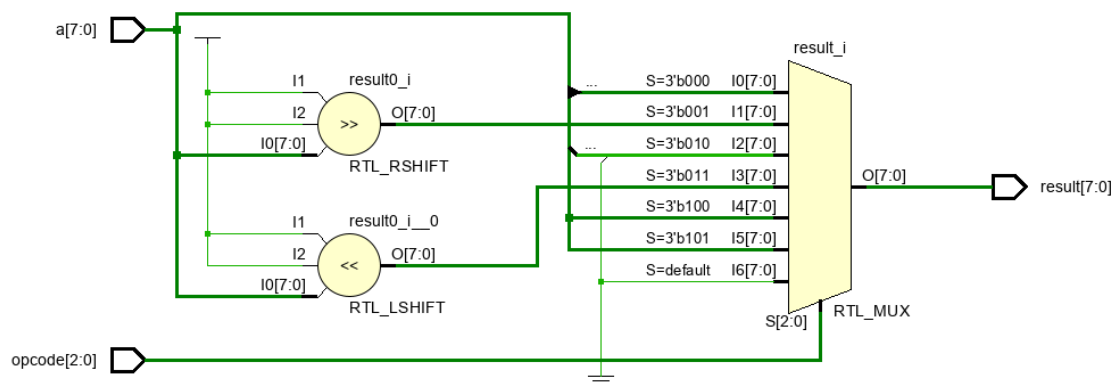

Synthesis Report:

Start Writing Synthesis Report

Report BlackBoxes:

BlackBox name	Instances

Report Cell Usage:

Cell	Count
LUT5	7
LUT6	1
IBUF	11
OBUF	8

Report Instance Areas:

Instance	Module	Cells
top		27

Finished Writing Synthesis Report : Time (s): cpu = 00:00:23 ; elapsed = 00:00:33 . Memory (MB): peak = 1017.926 ; gain = 0.000


Power Report:

Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power:	3.055 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	30.8°C
Thermal Margin:	54.2°C (28.6 W)
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

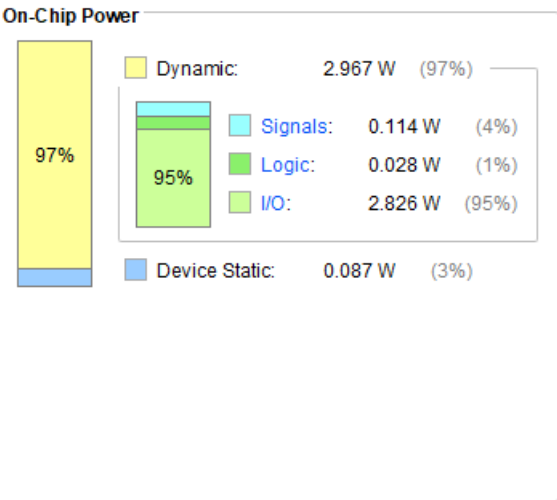[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



Q8. ALU

Verilog Code:

```
.....  
module alu (a, b, opcode, rslt);  
  
input [3:0] a, b;  
input [2:0] opcode;  
output [7:0] rslt;  
  
reg [7:0] rslt;  
  
parameter add_op = 3'b000,  
sub_op = 3'b001,  
mul_op = 3'b010,  
and_op = 3'b011,  
or_op = 3'b100,  
not_op = 3'b101,  
xor_op = 3'b110,  
xnor_op = 3'b111;  
  
always @ (a or b or opcode)  
begin  
case (opcode)  
add_op: rslt = a + b;  
sub_op: rslt = a - b;  
mul_op: rslt = a * b;  
and_op: rslt = a & b; //also ab  
or_op: rslt = a | b;  
not_op: rslt = ~a; //also ~b  
xor_op: rslt = a ^ b;  
xnor_op: rslt = ~(a ^ b);  
endcase  
end  
endmodule
```

```

`timescale 1ns / 1ps
module alu_tb;
    reg [3:0] a;
    reg [3:0] b;
    reg [2:0] opcode;
    wire [7:0] rslt;
    alu uut (.a(a), .b(b), .opcode(opcode), .rslt(rslt));
    initial
    begin
        #0 a = 4'b0001; b = 4'b0010; opcode = 3'b000;
        #10 a = 4'b0110; b = 4'b0110; opcode = 3'b000;
        #10 a = 4'b1100; b = 4'b0011; opcode = 3'b001;
        #10 a = 4'b1101; b = 4'b1010; opcode = 3'b001;
        #10 a = 4'b1100; b = 4'b0111; opcode = 3'b010;
        #10 a = 4'b1111; b = 4'b0011; opcode = 3'b010;
        #10 a = 4'b1100; b = 4'b0111; opcode = 3'b011;
        #10 a = 4'b1101; b = 4'b1011; opcode = 3'b011;
        #10 a = 4'b0101; b = 4'b1011; opcode = 3'b100;
        #10 a = 4'b1001; b = 4'b1010; opcode = 3'b100;
        #10 a = 4'b1001; opcode = 3'b101;
        #10 a = 4'b0011; opcode = 3'b101;
        #10 a = 4'b0111; b = 4'b1011; opcode = 3'b110;
        #10 a = 4'b1010; b = 4'b0101; opcode = 3'b110;
        #10 a = 4'b0110; b = 4'b0110; opcode = 3'b111;
        #10 a = 4'b0011; b = 4'b1110; opcode = 3'b111;
    end
    initial
    begin
        $monitor(" A=%b | B=%b | Opcode = %b | Result=%b",a,b,opcode,rslt);
        #300 $finish;
    end
endmodule

```

The diagram illustrates the RTL implementation of a 7-bit ALU. It features several input registers: `a[3:0]`, `b[3:0]`, and `opcode[2:0]`. The ALU performs various operations based on the `opcode` value, which is decoded by a 3-to-8 decoder (labeled `s[2:0]`). The operations include addition (`RTL_ADD`), subtraction (`RTL_SUB`), multiplication (`RTL_MULT`), bitwise AND (`RTL_AND`), bitwise OR (`RTL_OR`), and bitwise inversion (`RTL_INV`). The results of these operations are stored in registers `rslt0_i_0` through `rslt0_i_6`. The final 7-bit result, `rslt[7:0]`, is selected from these registers by a multiplexer (`RTL_MUX`).

Synthesis Report:

Start Writing Synthesis Report

Report BlackBoxes:

BlackBox name	Instances
---------------	-----------

Report Cell Usage:

Cell	Count
CARRY4	2
LUT2	6
LUT4	6
LUT5	7
LUT6	19
MUXF7	3
IBUF	11
OBUF	8

Report Instance Areas:

Instance	Module	Cells
top		62

Finished Writing Synthesis Report : Time (s): cpu = 00:00:17 ; elapsed = 00:00:21 . Memory (MB): peak = 1016.625 ; gain = 0.000

Power Report:

Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power:

4.409 W

Design Power Budget:

Not Specified

Power Budget Margin:

N/A

Junction Temperature:

33.3°C

Thermal Margin:

51.7°C (27.3 W)

Effective θJA:

1.9°C/W

Power supplied to off-chip devices:

0 W

Confidence level:

Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

98%

Dynamic: 4.318 W (98%)

93%

Signals: 0.118 W (3%)

Logic: 0.168 W (4%)

I/O: 4.032 W (93%)

Device Static: 0.091 W (2%)

Q9. 4-BIT Asynchronous Down Counter

Verilog Code:

```
module dff(q,qbar,clk,rst,d);
    output reg q;
    output qbar;
    input clk, rst;
    input d;

    assign qbar = ~q;

    always @(posedge clk, posedge rst)
    begin
        if (rst)
            q <= 0;
        else
            q <= d;
        end
    endmodule

module async_counter(count,countbar,clk,rst);
    input clk, rst;
    output [3:0] count, countbar;
    dff dff1(count[0],countbar[0],clk,rst,countbar[0]);
    dff dff2(count[1],countbar[1],count[0],rst,countbar[1]);
    dff dff3(count[2],countbar[2],count[1],rst,countbar[2]);
    dff dff4(count[3],countbar[3],count[2],rst,countbar[3]);

endmodule
```

Test Bench:

```
module async_counter_tb;

    // Inputs
    reg clk;
    reg rst;


    // Outputs
    wire [3:0] count;
    wire [3:0] countbar;

    // Instantiate the Unit Under Test (UUT)
    async_counter uut (
        .count(count),
        .countbar(countbar),
        .clk(clk),
        .rst(rst)
    );

    initial
    begin
        clk = 0;
        rst = 1;
        #23; // Just give enough time to reset the design
        rst = 0;
        #200;
        $finish;
    end
    always #5 clk = ~clk;

endmodule
```

RTL Schematic:

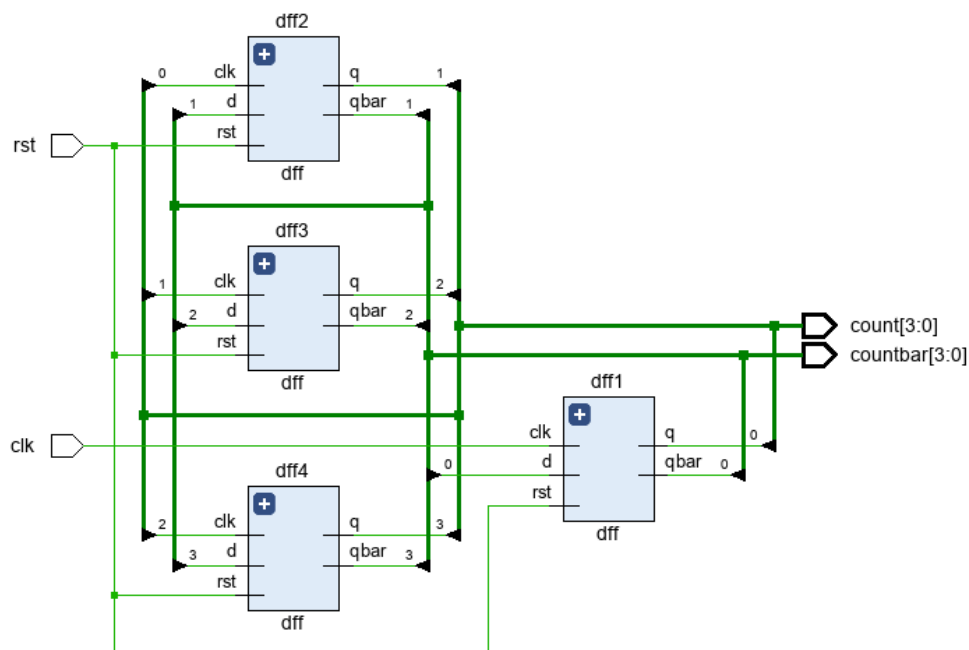

Synthesis Report:

Start Writing Synthesis Report		

Report BlackBoxes:		
+-----+		
BlackBox name Instances		
+-----+		
+-----+		
Report Cell Usage:		
+-----+		
Cell Count		
+-----+		
1 BUFG 1		
2 LUT1 4		
3 FDCE 4		
4 IBUF 2		
5 OBUF 8		
+-----+		
Report Instance Areas:		
+-----+		
Instance Module Cells		
+-----+		
1 top 19		
2 dff1 dff_0 2		
3 dff2 dff_0 2		
4 dff3 dff_1 2		
5 dff4 dff_2 2		
+-----+		

Finished Writing Synthesis Report : Time (s): cpu = 00:00:27 ; elapsed = 00:00:37 . Memory (MB): peak = 1017.906 ; gain = 0.000		

Power Report:

Summary	
Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.	
Total On-Chip Power:	16.203 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	55.5°C
Thermal Margin:	29.5°C (15.5 W)
Effective θJA:	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low
Launch Power Constraint Advisor to find and fix invalid switching activity	
On-Chip Power	
<div><div><div>99%</div></div><div><div>Dynamic: 16.062 W (99%)</div><div><div>94%</div><div>Signals: 0.781 W (5%)</div><div>Logic: 0.074 W (1%)</div><div>I/O: 15.207 W (94%)</div></div><div>Device Static: 0.141 W (1%)</div></div></div>	

Q10. MOD-N Up-down Counter


Verilog Code:

```
`timescale 1ns / 1ps
| module modN_counter
|     # (parameter N = 10,
|         parameter WIDTH = 4)
|
|     ( input  clk,
|       input  reset,
|       input  upordown,
|       output reg[WIDTH-1:0] count);
|
|     always @ (posedge clk )
|     begin
|         if (reset==1)
|             count <= 0;
|
|         else
|             if(upordown==1)          //Up Mode is selected
|                 if (count == N-1)
|                     count <= 0;
|                 else
|                     count<=count+1; //increment counter
|
|             else                      //Down Mode is selected
|                 if(count==0)
|                     count<=N-1;
|                 else
|                     count<=count-1; //Decrement the counter
|
|     end
| endmodule
```

Test Bench:

```
`timescale 1ns / 1ps
module modN_updown_tb;
    reg clk;
    reg reset;
    reg upordown;
    wire [3:0] count;
    modN_counter uut (
        .clk(clk),
        .reset(reset),
        .upordown(upordown),
        .count(count)
    );
    initial begin
        clk = 0;
        reset = 1;
        #50 reset = 0; upordown = 0;
        #200;
        upordown = 1;
        #200;
        reset = 1;
        upordown = 0;
        #100;
        reset = 0;
    end
    always #10 clk=~clk;
    initial
    begin
        $monitor("UporDown=%b | Count=%b",upordown,count);
        #1000 $finish;
    end
endmodule
```

RTL Schematic:

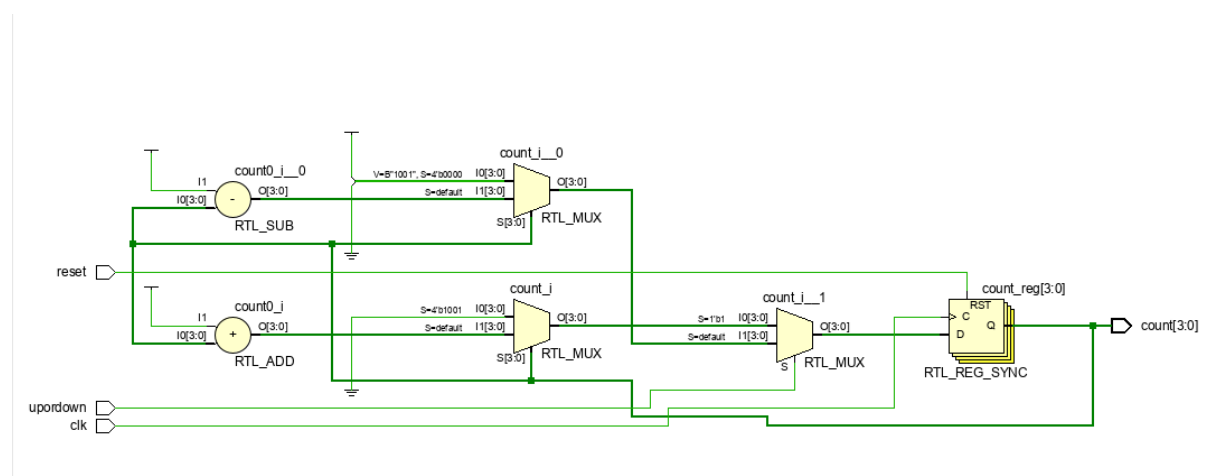

Synthesis Report:

Start Writing Synthesis Report

Report BlackBoxes:

BlackBox name	Instances

Report Cell Usage:

Cell	Count
1	BUFG 1
2	LUT1 1
3	LUT5 3
4	FDRE 4
5	IBUF 3
6	OBUF 4

Report Instance Areas:

Instance	Module	Cells
1	top	16

Finished Writing Synthesis Report : Time (s): cpu = 00:00:18 ; elapsed = 00:00:22 . Memory (MB): peak = 1015.855 ; gain = 0.000

Power Report:

Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power:

3.805 W

Design Power Budget:

Not Specified

Power Budget Margin:

N/A

Junction Temperature:

32.2°C

Thermal Margin:

52.8°C (27.9 W)

Effective SJA:

1.9°C/W


Power supplied to off-chip devices:

0 W

Confidence level:

Low

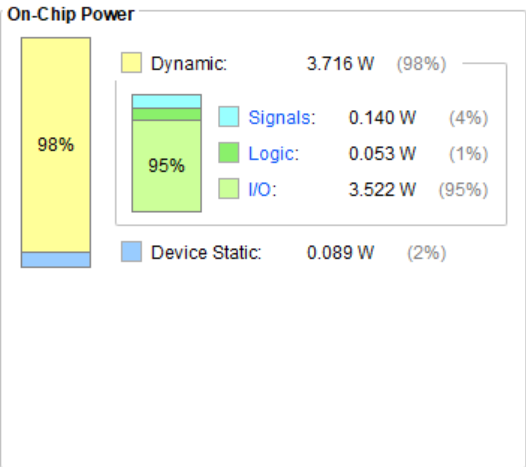[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



Q11. Universal Binary Counter


Verilog Code:

```
`timescale 1ns / 1ps
module univ_bin_counter
#(parameter N=8)
(
    input wire clk, reset,
    input wire syn_clr, load, en, up,
    input wire [N-1:0] d,
    output wire max, min,
    output wire [N-1:0] q
);
    reg [N-1:0] r_reg, r_next;
    always @(posedge clk, posedge reset)
    if (reset)
        r_reg <= 0; //
    else
        r_reg <= r_next;
    always @(*)
    if (syn_clr)
        r_next = 0;
    else if (load)
        r_next = d;
    else if (en & up)
        r_next = r_reg + 1;
    else if (en & ~up)
        r_next = r_reg - 1;
    else
        r_next = r_reg;
    assign q = r_reg;
    assign max = (r_reg==2**N-1) ? 1'b1 : 1'b0;
    assign min = (r_reg==0) ? 1'b1 : 1'b0;
endmodule
```

Test Bench:

```
`timescale 1ns / 1ps
module univ_bin_counter_tb;
    reg clk;
    reg reset;
    reg syn_clr;
    reg load;
    reg en;
    reg up;
    reg [7:0] d;
    wire max;
    wire min;
    wire [7:0] q;
    univ_bin_counter uut (.clk(clk), .reset(reset), .syn_clr(syn_clr), .load(load), .en(en), .up(up), .d(d), .max(max), .min(min), .q(q));
    initial begin
        clk = 0;
        reset = 0;
        syn_clr = 0;
        load = 0;
        en = 0;
        up = 0;
        d = 0;
        #10 reset = 1; syn_clr = 1; load = 1; en = 1; up = 1; d = 1;
        #10 reset = 0; syn_clr = 0; load = 1; en = 1; up = 1; d = 1;
        #10 reset = 0; syn_clr = 0; load = 0; en = 1; up = 1; d = 1;
        #400 reset = 0; syn_clr = 0; load = 0; en = 1; up = 0; d = 1;
    end
    always #5 clk = ~clk;
    initial
    begin
        $monitor(" Reset=%b | Sync_clr=%b | Load=%b | En=%b | Up=%b | D=%b | Q=%b", reset, syn_clr, load, en, up, d, q);
        #1000 $finish;
    end
endmodule
```

RTL Schematic:

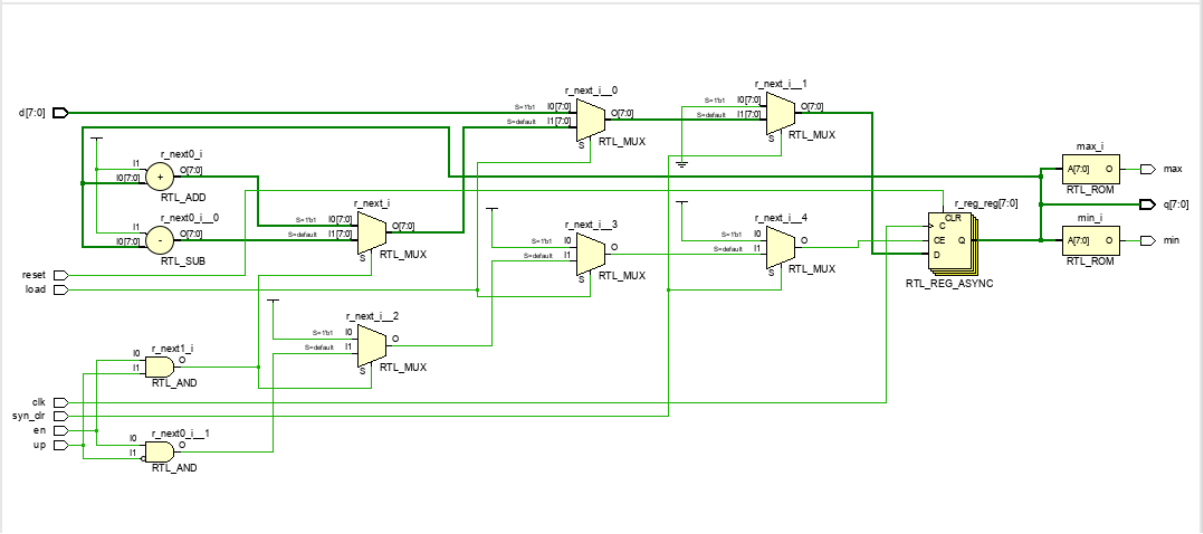

Synthesis Report:

Start Writing Synthesis Report

Report BlackBoxes:
+-----+
| BlackBox name | Instances |
+-----+
+-----+

Report Cell Usage:
+-----+
| Cell | Count |
+-----+
1	BUFG	1
2	CARRY4	2
3	LUT1	1
4	LUT2	6
5	LUT3	2
6	LUT4	10
7	LUT5	2
8	FDCE	8
9	IBUF	14
10	OBUF	10
+-----+

Report Instance Areas:
+-----+
| Instance | Module | Cells |
+-----+
|1 |top | | 56|
+-----+

Finished Writing Synthesis Report : Time (s): cpu = 00:00:26 ; elapsed = 00:00:34 . Memory (MB): peak = 1019.758 ; gain = 0.000

Power Report:

Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power:	3.709 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	32.0°C
Thermal Margin:	53.0°C (28.0 W)
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

98%

Dynamic: 3.620 W (98%)

94%

Signals: 0.123 W (3%)

Logic: 0.122 W (3%)

I/O: 3.375 W (94%)

Device Static: 0.089 W (2%)

Q12. Universal Shift Register

Verilog Code:


```
`timescale 1ns / 1ps
module universal_shiftreg(DATAOUT, clock, reset, MODE, DATAIN);
    output reg [3:0] DATAOUT;
    input clock, reset;
    input [1:0] MODE;
    input [3:0] DATAIN;

    always @(posedge clock)
    begin
        if(reset)
            DATAOUT <= 0;
        else
            begin
                case (MODE)
                    2'b00 : DATAOUT <= DATAOUT;    // locked mode, do nothing
                    2'b01 : DATAOUT <= {DATAIN[0], DATAIN[3:1]}; // DATAOUT >> 1;
                    2'b10 : DATAOUT <= {DATAIN[2:0], DATAIN[3]}; // DATAOUT << 1;
                    2'b11 : DATAOUT <= DATAIN;      // parallel in parallel out
                endcase
            end
        end
    end
endmodule
```

Test Bench:

```
`timescale 1ns / 1ps
module univ_bin_counter_tb;
    reg clk;
    reg reset;
    reg syn_clr;
    reg load;
    reg en;
    reg up;
    reg [7:0] d;
    wire max;
    wire min;
    wire [7:0] q;
    univ_bin_counter uut (.clk(clk), .reset(reset), .syn_clr(syn_clr), .load(load), .en(en), .up(up), .d(d), .max(max), .min(min), .q(q));
    initial begin
        clk = 0;
        reset = 0;
        syn_clr = 0;
        load = 0;
        en = 0;
        up = 0;
        d = 0;
        #10 reset = 1; syn_clr = 1; load = 1; en = 1; up = 1; d = 1;
        #10 reset = 0; syn_clr = 0; load = 1; en = 1; up = 1; d = 1;
        #10 reset = 0; syn_clr = 0; load = 0; en = 1; up = 1; d = 1;
        #400 reset = 0; syn_clr = 0; load = 0; en = 1; up = 0; d = 1;
    end
    always #5 clk = ~clk;
    initial
    begin
        $monitor(" Reset=%b | Sync_clr=%b | Load=%b | En=%b | Up=%b | D=%b | Q=%b", reset, syn_clr, load, en, up, d, q);
        #1000 $finish;
    end
endmodule
```

RTL Schematic:

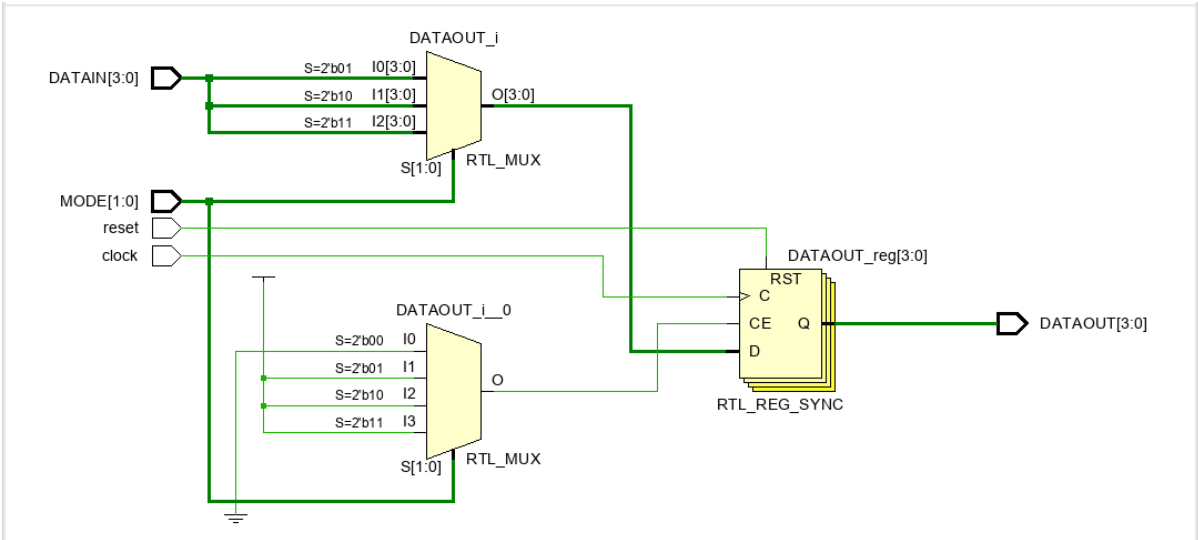

Synthesis Report:

Start Writing Synthesis Report

Report BlackBoxes:

BlackBox name	Instances

Report Cell Usage:

Cell	Count
BUFG	1
LUT2	1
LUT5	4
FDRE	4
IBUF	8
OBUF	4

Report Instance Areas:

Instance	Module	Cells
1	top	22

Finished Writing Synthesis Report : Time (s): cpu = 00:00:25 ; elapsed = 00:00:35 . Memory (MB): peak = 1017.617 ; gain = 0.000


Power Report:

Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power:	1.333 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	27.5°C
Thermal Margin:	57.5°C (30.3 W)
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

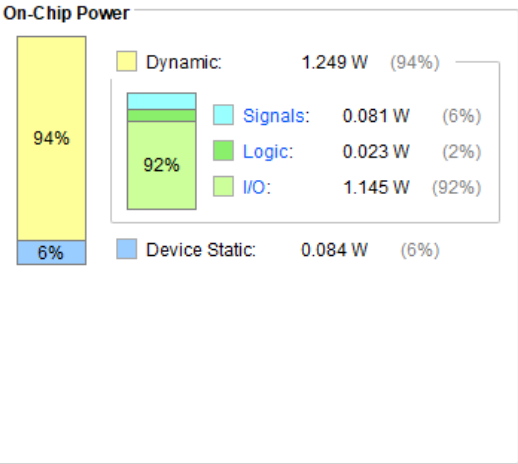[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



Q13. CN(Change-No Change Flip-Flop) using 2:1 MUX

Verilog Code:

```
module mux2X1(a,b,s,y);
input a,b,s;
output reg y;
always @(a or b or s)
begin
case(s)
0: y=a;
1:y=b;
default: y=1'b0;
endcase
end
endmodule

module d_ff(d,clk,reset,q);
input d,clk,reset;
output reg q;
always @(posedge clk)
begin
if(reset)
q=0;
else
q=d;
end
endmodule

module cn_flipflop(c,n,clk,q,qbar);
input c,n,clk;
output q,qbar;
wire cn,n_bar,d_wire;
mux2X1 mux1(1'b0,c,n,cn);
mux2X1 mux2(1'b1,1'b0,n,n_bar);
mux2X1 mux3(cn,n_bar,q,d_wire);
d_ff dff1(.d(d_wire),.clk(clk),.reset(),.q(q));
assign qbar=~q;
endmodule
```

Test Bench:


```
`timescale 1ns / 1ps
module cn_flipflop_tb;

    reg c;
    reg n;
    reg clk;
    wire q,qbar;

    cn_flipflop uut (.c(c),.n(n),.clk(clk),.q(q),.qbar(qbar));

    initial begin
        c = 0;
        n = 0;
        clk = 0;
        #10 c=0;n=1;
        #10 c=1;n=0;
        #10 c=1;n=1;
    end
    always #5 clk=~clk;
    initial
    begin $monitor("C=%b | N=%b | Q=%b | Qbar=%b",c,n,q,qbar);
        #100 $finish;
    end
endmodule
```

RTL Schematic:

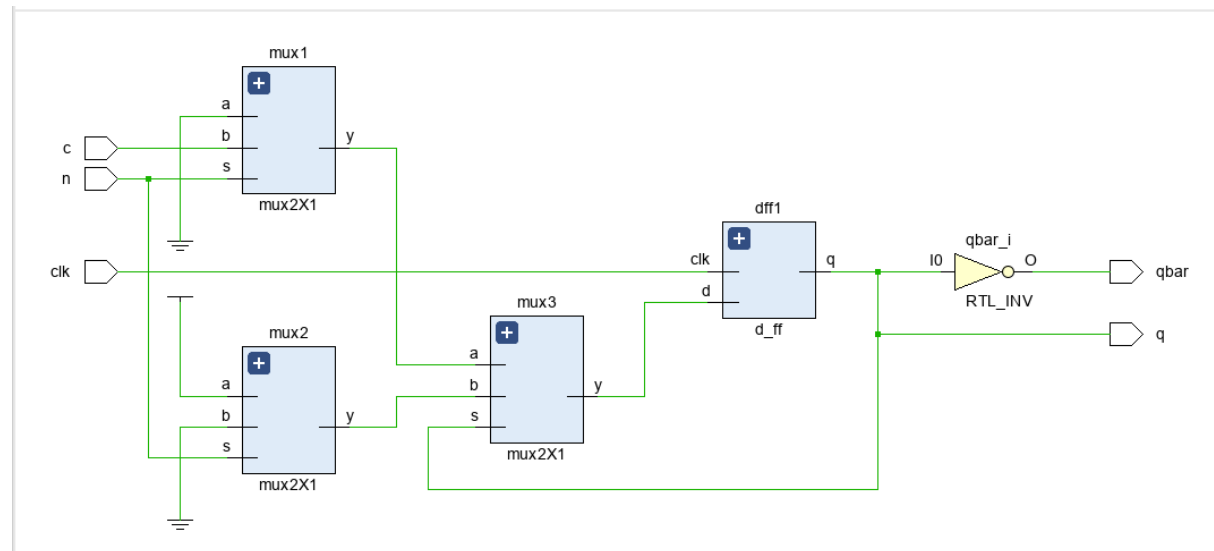

Synthesis Report:

Start Writing Synthesis Report

Report BlackBoxes:

BlackBox name	Instances

Report Cell Usage:

Cell	Count
BUFG	1
LUT1	1
LUT3	1
FDRE	1
IBUF	3
OBUF	2

Report Instance Areas:

Instance	Module	Cells
top		9
dff1	d_ff	3

Finished Writing Synthesis Report : Time (s): cpu = 00:00:24 ; elapsed = 00:00:34 . Memory (MB): peak = 1014.594 ; gain = 0.000

Power Report:

Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power:	0.856 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	26.6°C
Thermal Margin:	58.4°C (30.8 W)
Effective θJA:	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

Dynamic:	0.773 W	(90%)
Signals:	0.023 W	(3%)
Logic:	0.012 W	(2%)
I/O:	0.738 W	(95%)
Device Static:	0.083 W	(10%)

Q14.Frequency Divider by Odd Numbers

Verilog Code:

```
`timescale 1ns / 1ps
module clk_div_odd
#(parameter N=5)
( input  clk_in,output  clk_out);

    reg  [3:0] count = 4'b0;
    reg      A1 = 0;
    reg      B1 = 0;
    reg      Tff_A = 0;
    reg      Tff_B = 0;
    wire      clock_out;
    wire      wTff_A;
    wire      wTff_B;
    assign     wTff_A  = Tff_A;
    assign     wTff_B  = Tff_B;

    assign     clk_out = wTff_B ^ wTff_A;
always@(posedge clk_in)
begin
    if(count == N-1)
    begin
        count <= 4'b0000;
    end
    else
    begin
        count <= count + 1;
    end
end
always@(posedge clk_in)
begin
    if(count == 4'b0000)
        A1 <= 1;
    else
        A1 <= 0;
    end
end
```



```

|     A1 <= 0;
| end
| always@(posedge clk_in)
| begin
|     if(count == (N+1)/2)
|         B1 <= 1;
|     else
|         B1 <= 0;
|     end
| always@(negedge A1)
| begin
|     Tff_A <= ~Tff_A;
| end

| always@(negedge clk_in)
| begin
|     if(B1)
|         begin
|             Tff_B <= ~Tff_B;
|         end
|     end
| end
| endmodule

```

Test Bench:

```

`timescale 1ns / 1ps
) module clk_div_odd_tb;
    reg clk_in;
    wire clk_out;
    clk_div_odd uut (
        .clk_in(clk_in),
        .clk_out(clk_out)
    );

    initial begin
        clk_in=1;
    end


    always #10 clk_in= ~clk_in;

    initial
    #200 $finish;

) endmodule

```

RTL Schematic:

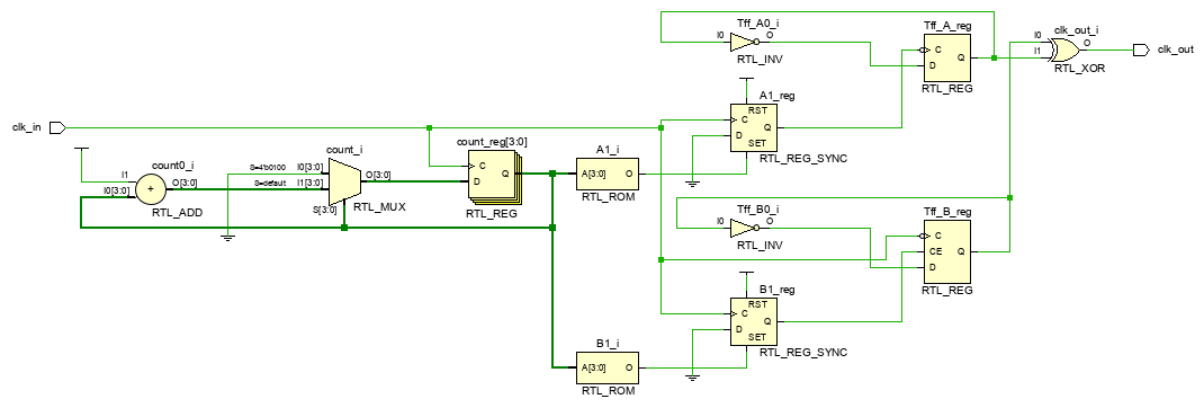

Synthesis Report:

Start Writing Synthesis Report

Report BlackBoxes:

BlackBox name	Instances

Report Cell Usage:

Cell	Count
BUFG	1
LUT1	2
LUT2	3
LUT3	1
LUT4	4
FDRE	8
IBUF	1
OBUF	1

Report Instance Areas:

Instance	Module	Cells
1	top	21

Finished Writing Synthesis Report : Time (s): cpu = 00:00:25 ; elapsed = 00:00:34 . Memory (MB): peak = 1015.637 ; gain = 0.000

Power Report:


Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power: 2.168 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 29.1°C
Thermal Margin: 55.9°C (29.5 W)
Effective θ_{JA} : 1.9°C/W
Power supplied to off-chip devices: 0 W
Confidence level: Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

 

Q15. Greatest Common Divisor using Behavioural Modelling

Verilog Code:

```
`timescale 1ns / 1ps
module gcd_beh #( parameter W = 4)
(
    input [W-1:0] A, B,
    input clk,rst,
    output reg [W-1:0] GCD
);
    reg [W-1:0] Ain, Bin;
always @(posedge clk or negedge rst)
begin
    Ain = A; Bin = B;
    while( Ain != Bin)
    begin
        if ( Ain < Bin )
            Bin = Bin-Ain;
        else
            Ain = Ain - Bin;
        end
        GCD = Ain;
    end
endmodule
```

Test Bench:

```
`timescale 1ns / 1ps
module gcd_beh_tb;
    parameter W=7;
    reg [W-1:0] A;
    reg [W-1:0] B;
    wire [W-1:0] GCD;
    gcd_beh uut (.A(A),.B(B),.GCD(GCD));
    initial begin
        A=90;B=86;
        #10 A=48; B=12;
        #10 A=65;B=4;
        #10 A=48;B=7;
        #10 A=8;B=2;
        #10 A=125;B=6;
        #10 A=85;B=76;
        #10 A=54;B=44;
        #10 A=95;B=32;
        #10 A=109;B=91;
        #10 A=75;B=34;
    end
    initial
    begin
        $monitor("A= %d | B=%d | GCD=%d", A,B,GCD);
        #200 $finish;
    end
endmodule
```

Q16.Single Port RAM

Verilog Code:

```
module single_port_ram
#(parameter addr_width = 6,
parameter data_width = 8,
parameter depth = 64)
(
    input [data_width-1:0] data,
    input [addr_width-1:0] addr,
    input we,clk,
    output [data_width-1:0] q
);

reg [data_width-1:0] ram [depth-1:0];

reg [addr_width-1:0] addr_reg;

always @(posedge clk)
begin
    if(we)
        ram[addr] <=data;
    else
        addr_reg <=addr;
    end
assign q= ram[addr_reg];
endmodule
```


Test Bench:

```

`timescale 1ns / 1ps
module single_port_ram_tb;
    parameter addr_width = 6;
    parameter data_width = 8;
    parameter depth = 64;
    reg [data_width-1:0] data;
    reg [addr_width:0] addr;
    reg we;
    reg clk;
    wire [data_width-1:0] q;
    single_port_ram uut (.data(data), .addr(addr), .we(we), .clk(clk), .q(q));
    initial begin
        clk=0;
        forever #5 clk=~clk;
    end
end
initial begin
    data=8'h01;
    addr=5'd0;
    we=1'b1;
    #10
    data=8'h02;
    addr=5'd1;
    #10;
    data=8'h03;
    addr=5'd2;
    #10;
    addr=5'd0;
    we=1'b0;
    #10;
    addr=5'd1;
    #10;
    addr=5'd2;
    #10;
end
endmodule

```

RTL Schematic:

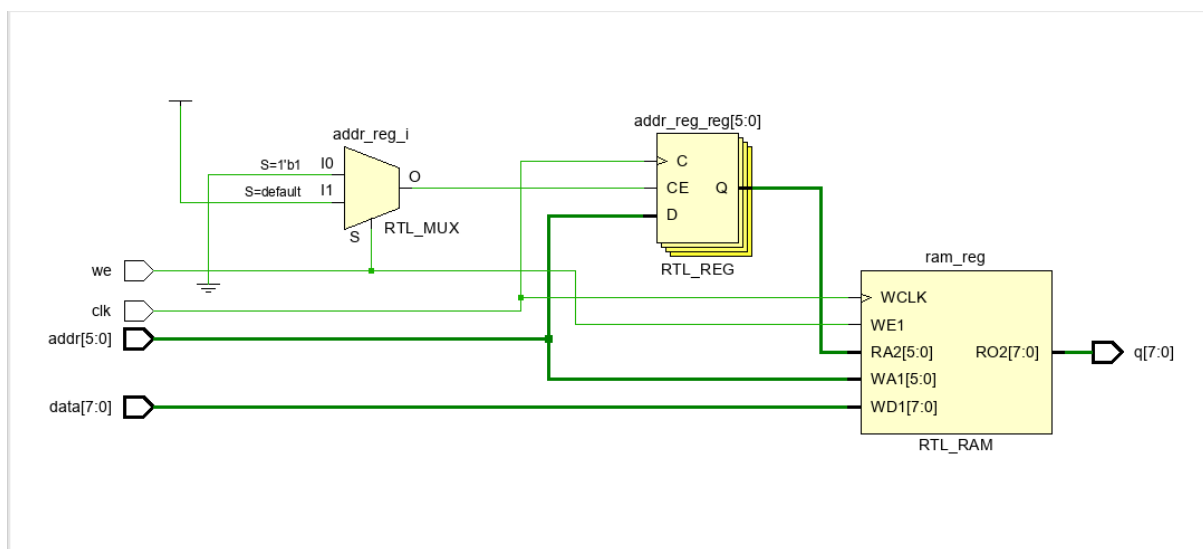

Synthesis Report:

Start Writing Synthesis Report

Report BlackBoxes:

BlackBox name	Instances

Report Cell Usage:

Cell	Count
BUFG	1
LUT1	1
RAM64M	2
RAM64X1D	2
FDRE	6
IBUF	16
OBUF	8

Report Instance Areas:

Instance	Module	Cells
top		36

Finished Writing Synthesis Report : Time (s): cpu = 00:00:13 ; elapsed = 00:00:18 . Memory (MB): peak = 1017.363 ; gain = 0.000


Power Report:

Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power:	2.194 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	29.1°C
Thermal Margin:	55.9°C (29.5 W)
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

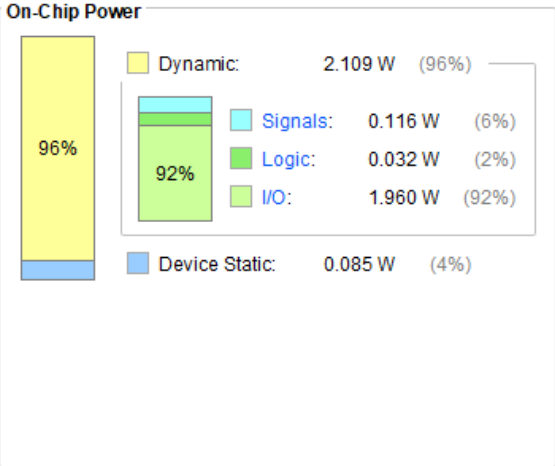[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



Q17. Dual Port RAM

Verilog Code:

```
module dual_port_ram
# (parameter data_width=8,
  parameter addr_width=4,
  parameter depth=16
)
(
  input clk,
  input wr_en,
  input [data_width-1:0] data_in,
  input [addr_width-1:0] addr_in_0,
  input [addr_width-1:0] addr_in_1,
  input port_en_0,
  input port_en_1,
  output [data_width-1:0] data_out_0,
  output [data_width-1:0] data_out_1
);

  reg [data_width-1:0] ram[0:depth-1];

always@(posedge clk)
begin
  if(port_en_0 == 1 && wr_en == 1)
    ram[addr_in_0] <= data_in;
end

assign data_out_0 = port_en_0 ? ram[addr_in_0] : 'dZ;
assign data_out_1 = port_en_1 ? ram[addr_in_1] : 'dZ;

endmodule
```


Test Bench:

```
module dual_port_ram_tb;
parameter addr_width = 4;
parameter data_width = 8;
parameter depth = 16;
integer i;
reg clk;
reg wr_en;
reg [data_width-1:0] data_in;
reg [addr_width-1:0] addr_in_0;
reg [addr_width-1:0] addr_in_1;
reg port_en_0;
reg port_en_1;
wire [data_width-1:0] data_out_0;
wire [data_width-1:0] data_out_1;
dual_port_ram uut (.clk(clk), .wr_en(wr_en), .data_in(data_in), .addr_in_0(addr_in_0), .addr_in_1(addr_in_1), .port_en_0(port_en_0), .port_en_1(port_en_1),
.data_out_0(data_out_0), .data_out_1(data_out_1));
always
#5 clk = ~clk;
initial begin
  clk = 1;
  addr_in_1 = 0;
  port_en_0 = 0;
  port_en_1 = 0;
  wr_en = 0;
  data_in = 0;
  addr_in_0 = 0;
  #20;
  port_en_0 = 1;
  wr_en = 1;
  for(i=1; i <= 16; i = i + 1) begin
    data_in = i;
    addr_in_0 = i-1;
    #10;
  end
  wr_en = 0;
```



```
        wr_en = 0;
        port_en_0 = 0;
        port_en_1 = 1;
        for(i=1; i <= 16; i = i + 1) begin
            addr_in_1 = i-1;
            #10;
        end
        port_en_1 = 0;
    end
endmodule
```

RTL Schematic:

 

Synthesis Report:

```
-----
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+
| BlackBox name | Instances |
+-----+
+-----+

Report Cell Usage:
+-----+
| Cell          | Count |
+-----+
|1| |BUFG|         | 1|
|2| |LUT1|        | 2|
|3| |LUT2|        | 1|
|4| |RAM16X1D|    | 8|
|5| |IBUF|        |20|
|6| |OBUFT|       |16|
+-----+

Report Instance Areas:
+-----+
| Instance | Module | Cells |
+-----+
|1| |top|   |    | 48|
+-----+

-----
Finished Writing Synthesis Report : Time (s): cpu = 00:00:14 ; elapsed = 00:00:20 . Memory (MB): peak = 1018.852 ; gain = 0.000
-----
```

Power Report:

Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power:	2.233 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	29.2°C
Thermal Margin:	55.8°C (29.4 W)
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

Dynamic:	2.147 W	(96%)
Device Static:	0.085 W	(4%)

Signals:	0.061 W	(3%)
Logic:	0.047 W	(2%)
I/O:	2.040 W	(95%)

Q18. Clock Buffer

Verilog Code:

```
`timescale 1ns / 1ps
module clock_buffer(mclk,bclk);
    input mclk;
    output bclk;
    buf b1(bclk,mclk);
endmodule
```

Test Bench:

```
`timescale 1ns / 1ps
module clock_buffer_tb();
    reg mclk;
    wire bclk;
    realtime t1,t2,t3,t4,t5,t6;
    parameter T=10;
    clock_buffer dut(mclk,bclk);
    initial
    begin
        mclk=1'b0;
        forever #(T/2) mclk=~mclk;
    end
    task master;
    begin
        @(posedge mclk) t1=$realtime;
        @(posedge mclk) t2=$realtime;
        t3=t2-t1;
    end
    endtask
    task bufout;
    begin
        @(posedge bclk) t4=$realtime;
        @(posedge bclk) t5=$realtime;
        t6=t5-t4;
    end
    endtask
    task freq_phase;
    realtime f,p;
    begin
        f=t6-t3;
        p=t4-t1;
        $display("freq_diff=%0t,phase_diff=%0t",f,p);
    end
    endtask
    initial
    begin
        fork master;
        bufout;
        join freq_phase;
    end
endmodule
```

RTL Schematic:



Synthesis Report:

```
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+
| BlackBox name |Instances |
+-----+
+-----+

Report Cell Usage:
+-----+
| Cell |Count |
+-----+
|1 |IBUF | 1|
|2 |OBUF | 1|
+-----+

Report Instance Areas:
+-----+
| Instance |Module |Cells |
+-----+
|1 |top | | 2|
+-----+

Finished Writing Synthesis Report : Time (s): cpu = 00:00:14 ; elapsed = 00:00:16 . Memory (MB): peak = 1015.395 ; gain = 0.000
```

Power Report:

Summary

Power estimation from Synthesized netlist. Activity derived from constraints files, simulation files or vectorless analysis. Note: these early estimates can change after implementation.

Total On-Chip Power:	0.333 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	25.6°C
Thermal Margin:	59.4°C (31.3 W)
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

75%

25%

Dynamic: 0.251 W (75%)

97%

Signals: 0.007 W (3%)

I/O: 0.244 W (97%)

Device Static: 0.082 W (25%)

Q19. Synchronous FIFO

Verilog Code:

```
module sync_fifo (input [7:0] data_in, input clk, rst, rd, wr,
output empty, full, output reg [3:0] fifo_cnt,
output reg [7:0] data_out);

    reg [7:0] fifo_ram [0:7];
    reg [2:0] rd_ptr, wr_ptr;
    assign empty= (fifo_cnt==0);
    assign full =(fifo_cnt==8);
    always @(posedge clk) begin: write
    if (wr && ! full)
        fifo_ram [wr_ptr] <= data_in;
    else if (wr && rd)
        fifo_ram [wr_ptr] <= data_in;
    end

    //Read and Write Clock
    always @ (posedge clk) begin: read
    if (rd && !empty)
        data_out <= fifo_ram [rd_ptr];
    else if (rd && wr)
        data_out <= fifo_ram [rd_ptr];
    end

    //pointer block
    always @(posedge clk) begin: pointer
    if (rst) begin
        wr_ptr <= 0;
        rd_ptr <= 0;
    end
    else begin
        wr_ptr <= ((wr && ! full) || (wr && rd)) ? wr_ptr+1 :
        wr_ptr;
    end
end
```

```

    wr_ptr;
    rd_ptr <= ((rd && !empty) || (wr && rd)) ? rd_ptr+1:
    rd_ptr;
end
end

//counter
always @(posedge clk) begin: count
    if (rst) fifo_cnt <= 0;
    else begin
        case ({wr, rd})
            2'b00: fifo_cnt <= fifo_cnt;
            2'b01: fifo_cnt <= (fifo_cnt==0) ? 0: fifo_cnt-1;
            2'b10: fifo_cnt <= (fifo_cnt==8) ? 8: fifo_cnt+1;
            2'b11 : fifo_cnt <= fifo_cnt;
            default: fifo_cnt <= fifo_cnt;
        endcase
    end
end
endmodule

```

Test Bench:

```
) module sync_fifo_tb();
  reg clk, rst, wr, rd ;
  reg[7:0] data_in;
  reg[7:0] tempdata;
  wire [7:0] data_out;
  wire [3:0] fifo_cnt;

  sync_fifo fifo( .clk(clk), .rst(rst), .data_in(data_in), .data_out(data_out),
    .wr(wr), .rd(rd), .empty(empty),
    .full(full), .fifo_cnt(fifo_cnt) );

) initial
) begin
  clk = 0;
  rst = 1;
  rd = 0;
  wr = 0;
  tempdata = 0;
  data_in = 0;

  #15 rst = 0;

  push(1);
  fork
    push(2);
    pop(tempdata);
  join
  push(10);
  push(20);
  push(30);
  push(40);
  push(50);
  push(60);
  push(70);
```

```
        push(70);
        push(80);
        push(90);
        push(100);
        push(110);
        push(120);
        push(130);

        pop(tempdata);
        push(tempdata);
        pop(tempdata);
        pop(tempdata);
        pop(tempdata);
        pop(tempdata);
        push(140);
        pop(tempdata);
        push(tempdata); //
        pop(tempdata);
        pop(tempdata);
        pop(tempdata);
        pop(tempdata);
        pop(tempdata);
        pop(tempdata);
        pop(tempdata);
        pop(tempdata);
        pop(tempdata);
        push(5);
        pop(tempdata);
    } end

    always
    #5 clk = ~clk;
```

```

always
    #5 clk = ~clk;

task push;
input[7:0] data;

    if( full )
        $display("---Cannot push: FIFO Full---");
    else
        begin
            $display("Pushed ",data );
            data_in = data;
            wr= 1;
            @(posedge clk);
            #1 wr = 0;
        end

endtask

task pop;
output [7:0] data;

    if( empty )
        $display("---Cannot Pop: FIFO Empty---");
    else
        begin

            rd = 1;
            @(posedge clk);

            #1 rd = 0;
            data = data_out;
            $display("-----Poped ", data);


```

```

    end
endtask
endmodule

```

RTL Schematic:

 

Synthesis Report:

Start Writing Synthesis Report

Report BlackBoxes:

```
+-----+
| BlackBox name | Instances |
+-----+
+-----+
```

Report Cell Usage:

	Cell	Count
1	BUFG	1
2	LUT2	3
3	LUT3	2
4	LUT4	4
5	LUT5	4
6	LUT6	4
7	RAM32M	2
8	FDRE	18
9	IBUF	12
10	OBUF	14

Report Instance Areas:

```

+-----+-----+-----+
|      |Instance|Module|Cells|
+-----+-----+-----+
|1      |top     |      |  64|
+-----+-----+-----+

```

Finished Writing Synthesis Report : Time (s): cpu = 00:00:14 ; elapsed = 00:00:16 . Memory (MB): peak = 1017.957 ; gain = 0.000

Power Report:


Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 3.239 W
Design Power Budget: Not Specified
Power Budget Margin: N/A
Junction Temperature: 31.1°C
Thermal Margin: 53.9°C (28.4 W)
Effective θ_{JA} : 1.9°C/W
Power supplied to off-chip devices: 0 W
Confidence level: Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

 

Q20. Priority Encoder


Verilog Code:

```
module pri_en(d,y,en);  
input [7:0] d;  
input en;  
output [2:0] y;  
reg [2:0] y;  
always @(d or en )  
begin  
if(en)  
begin  
casex(d)  
8'b00000001:y=3'b000;  
8'b0000001x:y=3'b001;  
8'b000001xx:y=3'b010;  
8'b00001xxx:y=3'b011;  
8'b0001xxxx:y=3'b100;  
8'b001xxxxx:y=3'b101;  
8'b01xxxxxx:y=3'b110;  
8'b1xxxxxxx:y=3'b111;  
endcase  
end  
else  
begin  
y=3'bxxx;  
end  
end  
endmodule
```

Test Bench:

```
module pri_en_tb();
  reg [7:0] d;
  reg en;
  wire [2:0] y;
  pri_en dut(d,y,en);
  initial
  begin
    en=1'b1;
    d=8'b00000001; #10;
    d=8'b00000011; #10;
    d=8'b00000101; #10;
    d=8'b00001001; #10;
    d=8'b00010001; #10;
    d=8'b00110001; #10;
    d=8'b01110001; #10;
    d=8'b11001001; #10;
    #10 d=8'b10111001;
    #10 d=8'b00101010;
    #10 d=8'b00000001;
    #10 d=8'b10100010;
  end
  initial
  $monitor("Input %8b | Output %3b | Enable %b ",d,y,en);
  initial #100 $finish;
endmodule
```

RTL Schematic:

 

Synthesis Report:

```
-----
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+
| BlackBox name |Instances |
+-----+
+-----+

Report Cell Usage:
+-----+
| Cell |Count |
+-----+
|1| LUT4 | 2|
|2| LUT5 | 2|
|3| LUT6 | 1|
|4| LD | 3|
|5| IBUF | 8|
|6| OBUF | 3|
+-----+

Report Instance Areas:
+-----+
| Instance |Module |Cells |
+-----+
|1| top | | 19|
+-----+

Finished Writing Synthesis Report : Time (s): cpu = 00:00:14 ; elapsed = 00:00:16 . Memory (MB): peak = 1018.668 ; gain = 0.000
-----
```

Power Report:

Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power:	0.158 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	25.3°C
Thermal Margin:	59.7°C (31.5 W)
Effective θJA:	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

Dynamic:	0.077 W	(49%)
Device Static:	0.081 W	(51%)

37%	Signals:	0.028 W	(37%)
18%	Logic:	0.014 W	(18%)
45%	I/O:	0.034 W	(45%)

Q21. Seven Segment Display using ROM

Verilog Code:

```
module ROM_sevenSegment
#(
    parameter addr_width = 16,
    addr_bits = 4,
    data_width = 7
)
(
    input wire [addr_bits-1:0] addr,
    output reg [data_width-1:0] data
);
always @*
begin
    case(addr)
        4'b0000 : data = 7'b1000000;
        4'b0001 : data = 7'b1111001;
        4'b0010 : data = 7'b0100100;
        4'b0011 : data = 7'b0110000;
        4'b0100 : data = 7'b0011001;
        4'b0101 : data = 7'b0010010;
        4'b0110 : data = 7'b0000010;
        4'b0111 : data = 7'b1111000;
        4'b1000 : data = 7'b0000000;
        4'b1001 : data = 7'b0010000;
        4'b1010 : data = 7'b0001000;
        4'b1011 : data = 7'b0000011;
        4'b1100 : data = 7'b1000110;
        4'b1101 : data = 7'b0100001;
        4'b1110 : data = 7'b0000110;
        default : data = 7'b0001110;
    endcase
end
endmodule
```

 

Test Bench:

```
`timescale 1ns / 1ps
module ROM_sevenSegment_Test
    ();
    reg [3:0] SW;
    wire [6:0] HEX0;
    wire [6:0] LEDR;

    integer i;
    wire [6:0] data;
    ROM_sevenSegment seven_segment_ROM(.addr(SW), .data(data));

    initial begin
    for(i=0;i<16;i=i+1)
    begin
        SW=i;
        #10;
    end
    end
    assign HEX0 = data;
    assign LEDR = data;
endmodule
```

RTL Schematic:



Synthesis Report:

```
-----
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+
| BlackBox name |Instances |
+-----+
+-----+

Report Cell Usage:
+-----+
| Cell |Count |
+-----+
|1     |LUT4  | 7|
|2     |IBUF  | 4|
|3     |OBUF  | 7|
+-----+

Report Instance Areas:
+-----+
| Instance |Module |Cells |
+-----+
|1         |top    |      | 18|
+-----+

-----
Finished Writing Synthesis Report : Time (s): cpu = 00:00:33 ; elapsed = 00:00:43 . Memory (MB): peak = 1018.848 ; gain = 0.000
-----
```


Power Report:

Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power:	2.649 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	30.0°C
Thermal Margin:	55.0°C (29.0 W)
Effective θ_{JA}:	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

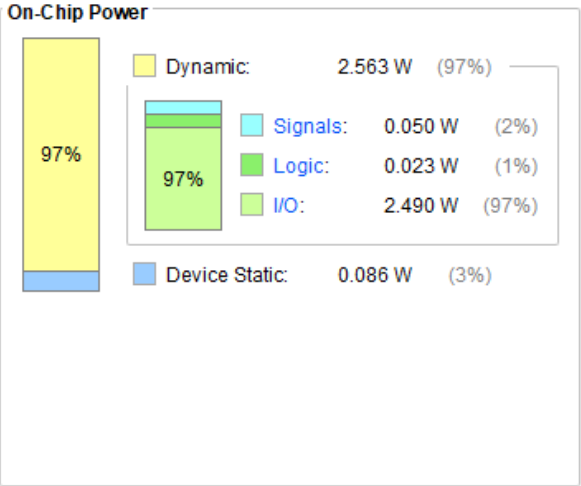[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



Q22. Serial Adder

Verilog Code:

```
`timescale 1ns / 1ps
module serial_adder
(
    input clk,reset,
    input a,b,cin,
    output reg s,cout
);

reg c,flag;


always@(posedge clk or posedge reset)
begin
    if(reset == 1) begin
        s = 0;
        cout = c;
        flag = 0;
    end else begin
        if(flag == 0)
        begin
            c = cin;
            flag = 1;
        end
        cout = 0;
        s = a ^ b ^ c;
        c = (a & b) | (c & b) | (a & c);
    end
end
endmodule
```

Test Bench:

```
module serial_adder_tb();
    reg clk;
    reg reset;
    reg a;
    reg b;
    reg cin;
    wire s;
    wire cout;
    serial_adder uut ( .clk(clk), .reset(reset), .a(a), .b(b), .cin(cin), .s(s), .cout(cout));
    always
        #5 clk = ~clk;
    initial begin
        clk = 1; reset = 0;
        a = 0; b = 0; cin = 0; reset = 1;
        #20;
        reset = 0;
        a = 1; b = 1; cin = 1;    #10;
        a = 1; b = 0; cin = 0;    #10;
        a = 1; b = 1; cin = 0;    #10;
        a = 1; b = 1; cin = 0;    #10;
        reset = 1;
        #10;
        reset = 0;

        a = 1; b = 1; cin = 1;    #10;
        a = 1; b = 0; cin = 0;    #10;
        a = 0; b = 0; cin = 0;    #10;
        a = 1; b = 0; cin = 0;    #10;
        a = 1; b = 1; cin = 0;    #10;
        reset = 1;
        #10;
    end
    initial $monitor(" A=%b | B=%b | Cin=%b | Sum=%b | Cout=%b | Clock =%b",a,b,cin,s,cout,clk);
endmodule
```

RTL Schematic:

 

Synthesis Report:

```
-----
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+
| BlackBox name |Instances |
+-----+
+-----+

Report Cell Usage:
+-----+
| Cell |Count |
+-----+
|1| BUFG | 1|
|2| LUT2 | 3|
|3| LUT5 | 1|
|4| LUT6 | 1|
|5| FDCE | 2|
|6| FDPE | 1|
|7| FDRE | 1|
|8| LDC | 1|
|9| IBUF | 5|
|10| OBUF | 2|
+-----+

Report Instance Areas:
+-----+
| Instance |Module |Cells |
+-----+
|1| top | | 18|
+-----+

-----
Finished Writing Synthesis Report : Time (s): cpu = 00:00:20 ; elapsed = 00:00:28 . Memory (MB): peak = 1014.773 ; gain = 0.000
-----
```

Power Report:

Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.618 W

Design Power Budget: Not Specified

Power Budget Margin: N/A

Junction Temperature: 26.2°C


Thermal Margin: 58.8°C (31.0 W)

Effective θ_{JA} : 1.9°C/W

Power supplied to off-chip devices: 0 W

Confidence level: Low

 [Launch Power Constraint Advisor](#) to find and fix invalid switching activity



Q23. Fixed Priority Arbiter

Verilog Code:

```
module fixedpriority_arbiter(output reg [3:0] GNT,  
    input [3:0] REQ,  
    input clk,reset  
);  
always @(posedge clk or negedge reset)  
// PRIORITY 3>1>0>2  
begin  
    if(!reset)  
        GNT<= 4'b0000;  
    else if(REQ[3])  
        GNT<= 4'b1000;  
    else if(REQ[1])  
        GNT<= 4'b0010;  
    else if(REQ[0])  
        GNT<= 4'b0001;  
    else if(REQ[2])  
        GNT<= 4'b0100;  
    else  
        GNT<= 4'b0000;  
    end  
endmodule
```

Test Bench:

```

`timescale 1ns / 1ps
module fixedpriority_arbiter_tb();
wire [3:0] GNT;

reg [3:0] REQ;
reg clk,reset ;


fixedpoint_arbiter dut(.GNT(GNT),.REQ(REQ),.clk(clk),.reset(reset));

initial
clk=0;
always #4 clk <= ~clk ;

initial
begin
reset =0;
#4 reset =1;
repeat(20)
begin
#5 REQ<=$random();
end
end
#100 $finish();
end
initial begin
$monitor("REQ=%b,GNT=%b,reset=%b",REQ,GNT,reset);
end
endmodule

```

RTL Schematic:

 

Synthesis Report:

```
-----
Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+
| BlackBox name |Instances |
+-----+
+-----+

Report Cell Usage:
+-----+
| Cell |Count |
+-----+
|1 |BUFG | 1|
|2 |LUT1 | 1|
|3 |LUT2 | 1|
|4 |LUT3 | 1|
|5 |LUT4 | 1|
|6 |FDCE | 4|
|7 |IBUF | 6|
|8 |OBUF | 4|
+-----+

Report Instance Areas:
+-----+
| Instance |Module |Cells |
+-----+
|1 |top | | 19|
+-----+

-----
Finished Writing Synthesis Report : Time (s): cpu = 00:00:25 ; elapsed = 00:00:35 . Memory (MB): peak = 1015.289 ; gain = 0.000
-----
```

Power Report:

Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power: 0.861 W

Design Power Budget: Not Specified

Power Budget Margin: N/A

Junction Temperature: 26.6°C


Thermal Margin: 58.4°C (30.8 W)

Effective θ_{JA} : 1.9°C/W

Power supplied to off-chip devices: 0 W

Confidence level: Low

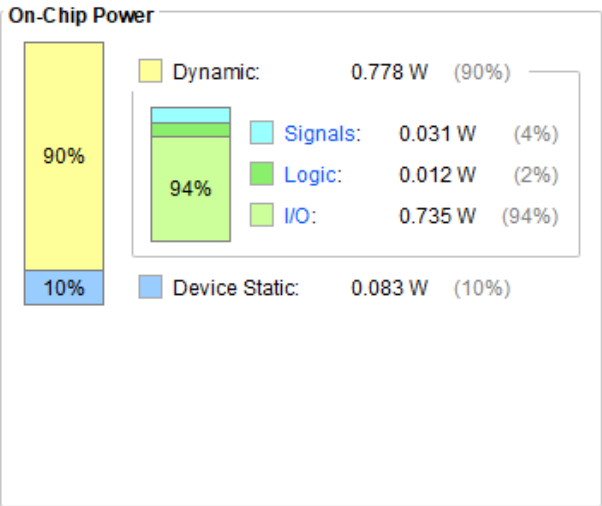[Launch Power Constraint Advisor](#) to find and fix invalid switching activity



Q24. Round Robin Arbiter

Verilog Code:

```
`timescale 1ns / 1ps
module roundrobin_arbiter(
    input clk,rst_n,
    input [3:0] REQ,
    output reg [3:0] GNT
);
    reg[2:0] pr_state;
    reg[2:0] nxt_state;

    parameter [2:0] Sideal = 3'b000;
    parameter [2:0] S0 = 3'b001;
    parameter [2:0] S1 = 3'b010;
    parameter [2:0] S2 = 3'b011;
    parameter [2:0] S3 = 3'b100;

    always @(posedge clk or negedge rst_n)

    begin
        if(!rst_n)
            pr_state <= Sideal;
        else
            pr_state <=nxt_state;
        end

    always@(*)
    begin
        case(pr_state)
            Sideal:
                begin
                    if(REQ[0])
                        nxt_state = S0;
                    else if (REQ[1])
                        nxt_state = S1;
                    else if (REQ[2])
                        nxt state = S2;
```

```
always@(*)
begin
    case(pr_state)
        Sideal:
            begin
                if(REQ[0])
                    nxt_state = S0;
                else if (REQ[1])
                    nxt_state = S1;
                else if (REQ[2])
                    nxt_state = S2;
                else if (REQ[3])
                    nxt_state = S3;
                else
                    nxt_state =Sideal;
            end
        S0:
            begin
                if (REQ[1])
                    nxt_state = S1;
                else if (REQ[2])
                    nxt_state = S2;
                else if (REQ[3])
                    nxt_state = S3;
                else if(REQ[0])
                    nxt_state =S0;
                else
                    nxt_state =Sideal;
            end
        S1:
            begin
                if (REQ[2])
                    nxt_state = S2;
                else if (REQ[3])
```

```

S1:
begin
    if (REQ[2])
        nxt_state = S2;
    else if (REQ[3])
        nxt_state = S3;
    else if (REQ[0])
        nxt_state = S0;
    else if (REQ[1])
        nxt_state = S1;
    else
        nxt_state = Sideal;
end

S2:
begin
    if (REQ[3])
        nxt_state = S3;
    else if (REQ[0])
        nxt_state = S0;
    else if (REQ[1])
        nxt_state = S1;
    else if (REQ[2])
        nxt_state = S2;
    else
        nxt_state = Sideal;
end

S3:
begin
    if (REQ[0])
        nxt_state = S0;
    else if (REQ[1])
        nxt_state = S1;
    else if (REQ[2])
        nxt_state = S2;
    else if (REQ[3])

```

```

        nxt_state = S2;
    else if (REQ[3])
        nxt_state = S3;
    else
        nxt_state = Sideal;
    end
endcase

end

always @(*)
begin
    case (pr_state)
        S0: GNT=4'b0001;
        S1: GNT=4'b0010;
        S2: GNT=4'b0011;
        S3: GNT=4'b0100;
        default: GNT=4'b0000;
    endcase
end
endmodule

```

Test Bench:

```

`timescale 1ns / 1ps
module roundrobin_arbiter_tb();
    reg clk;
    reg rst_n;
    reg [3:0] REQ;
    wire [3:0] GNT;
    roundrobin_arbiter DUT(.clk(clk), .rst_n(rst_n), .REQ(REQ), .GNT(GNT));

    always #5 clk = ~clk;
    initial begin
        clk = 0;
        rst_n = 1;
        REQ = 4'b0;
        #5 rst_n = 1;
        @(negedge clk) REQ = 4'b1000;
        @(negedge clk) REQ = 4'b1010;
        @(negedge clk) REQ = 4'b0010;
        @(negedge clk) REQ = 4'b0110;
        @(negedge clk) REQ = 4'b1110;
        @(negedge clk) REQ = 4'b1111;
        @(negedge clk) REQ = 4'b0100;
        @(negedge clk) REQ = 4'b0010;
        #5 rst_n = 0;
        #100 $finish;
    end
endmodule

```

```

Start Writing Synthesis Report
-----

Report BlackBoxes:
+-----+
| BlackBox name | Instances |
+-----+
+-----+

Report Cell Usage:
+-----+
| Cell | Count |
+-----+
|1| BUFG | 1|
|2| LUT1 | 1|
|3| LUT2 | 2|
|4| LUT3 | 2|
|5| LUT5 | 1|
|6| LUT6 | 4|
|7| MUXF7 | 2|
|8| FDCE | 3|
|9| IBUF | 6|
|10| OBUF | 4|
+-----+

Report Instance Areas:
+-----+
| Instance | Module | Cells |
+-----+
|1| top | | 26|
+-----+

Finished Writing Synthesis Report : Time (s): cpu = 00:00:19 ; elapsed = 00:00:25

```

Power Report:

Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

Total On-Chip Power:	1.408 W
Design Power Budget:	Not Specified
Power Budget Margin:	N/A
Junction Temperature:	27.7°C
Thermal Margin:	57.3°C (30.3 W)
Effective θ_{JA} :	1.9°C/W
Power supplied to off-chip devices:	0 W
Confidence level:	Low

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

On-Chip Power

The chart shows the power breakdown for On-Chip Power. The main bar is yellow, representing Dynamic power at 94%. A smaller blue bar at the bottom represents Device Static power at 6%. A callout box for the Dynamic power section shows a further breakdown: I/O (light green, 92%), Logic (dark green, 4%), and Signals (cyan, 4%).

Dynamic:	1.325 W	(94%)
Device Static:	0.084 W	(6%)
Signals:	0.059 W	(4%)
Logic:	0.051 W	(4%)
I/O:	1.215 W	(92%)